

# I Made my own Audio Bluetooth module

There are a lot of cheap audio bluetooth IC available in cheap these days. I got a bunch of them and here is my project.

 ElectroBoy

Follow project

Like project

Join this project 

6.4k

views

3

comments

670

followers

12

likes

- Description
- Details
- Files 3
- Components 0
- Logs 0
- Instructions 0
- Discussion 3

View Gallery

 6.4k  3  670  12

TEAM (1)

 ElectroBoy

Join this project's team

COMPLETED PROJECT

HARDWARE

---

## RELATED LISTS

### Favorites

A list of my favorite projects

---

This project was created on 03/24/2022 and last updated a year ago.

---


## DESCRIPTION

Hi guys, I am working with Bluetooth audio modules, chips and cards Since 2021. And finally, I tried to release my own version of Bluetooth module. Today's Bluetooth chips are very chip and integrated. I got my hands on some JL series Bluetooth chips, these are made in China and doesn't offer any kind of datasheets.

---


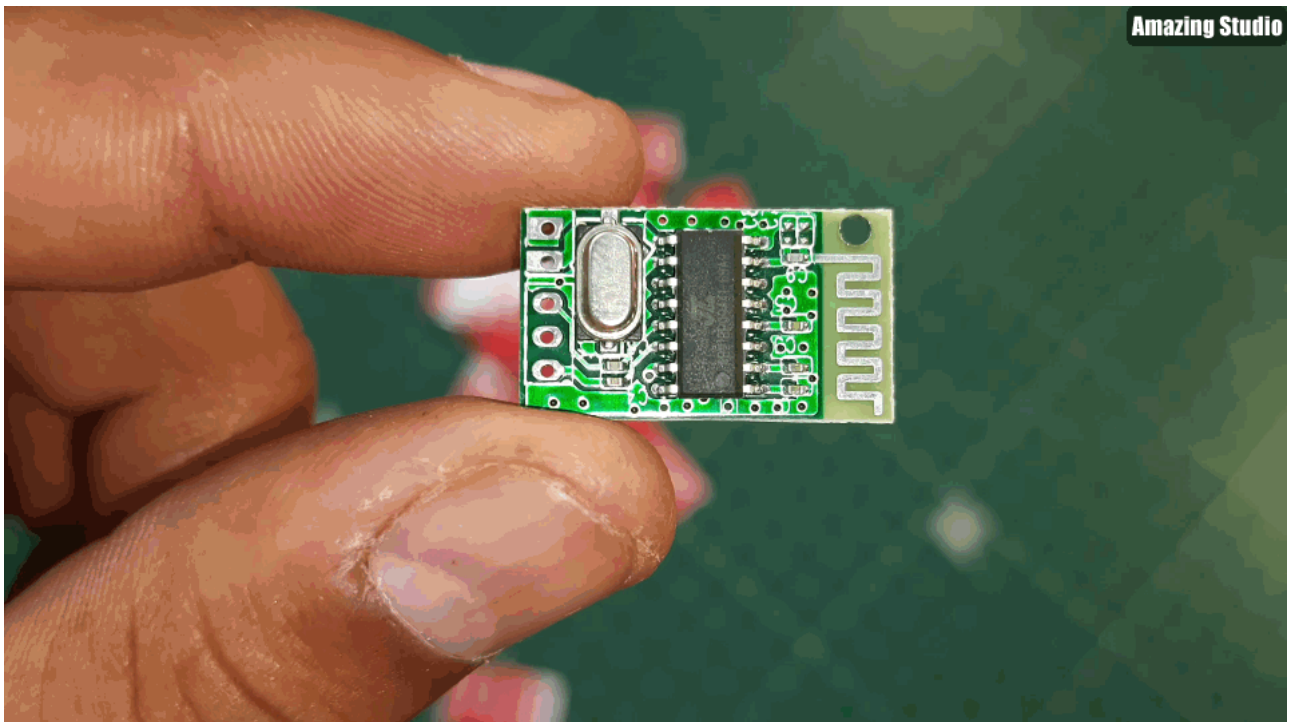
## DETAILS

Hi guys, I am working with Bluetooth audio modules, chips and cards Since 2021. And finally, I tried to release my own version of Bluetooth module. Today's Bluetooth chips are very chip and integrated. I got my hands on some JL series Bluetooth chips, these are made in China and doesn't offer any kind of datasheets.




But searching a little bit more on internet, I found some circuits and IC package details. Which are similar to my version JL\_AC6939B\_SOP16. I cross checked all the connections through datasheet and Bluetooth module that I have. Let's make the compatible circuit and order some of them from JLCPCB.

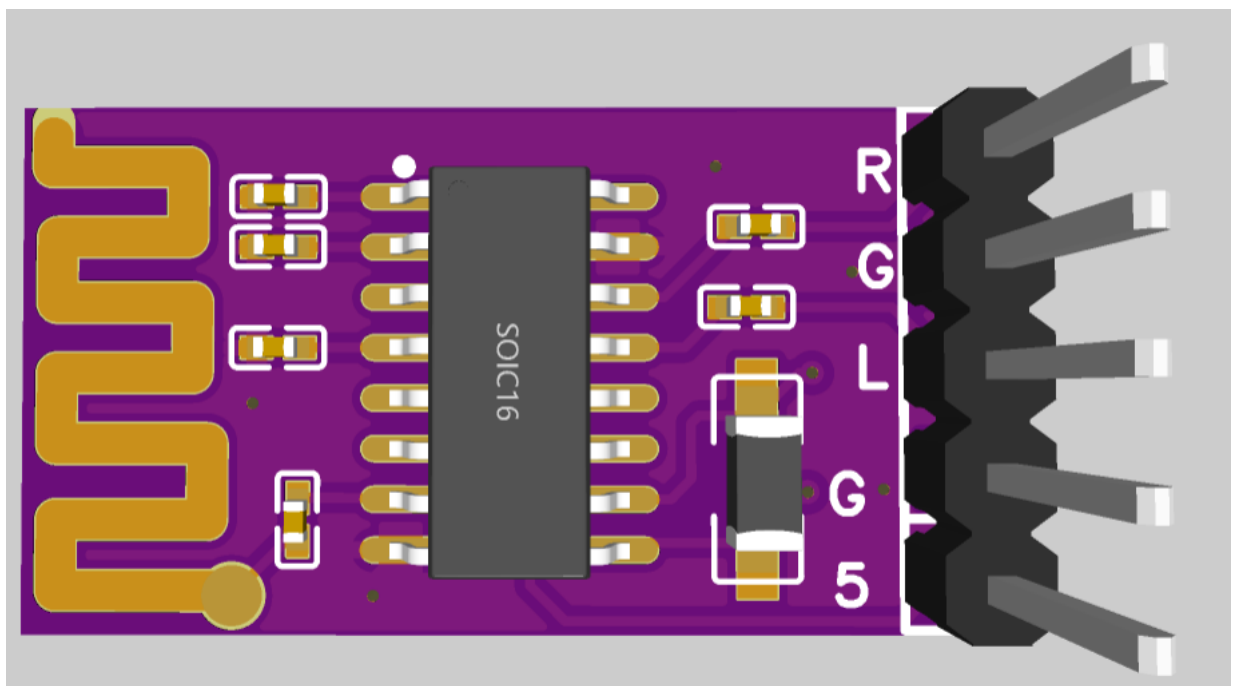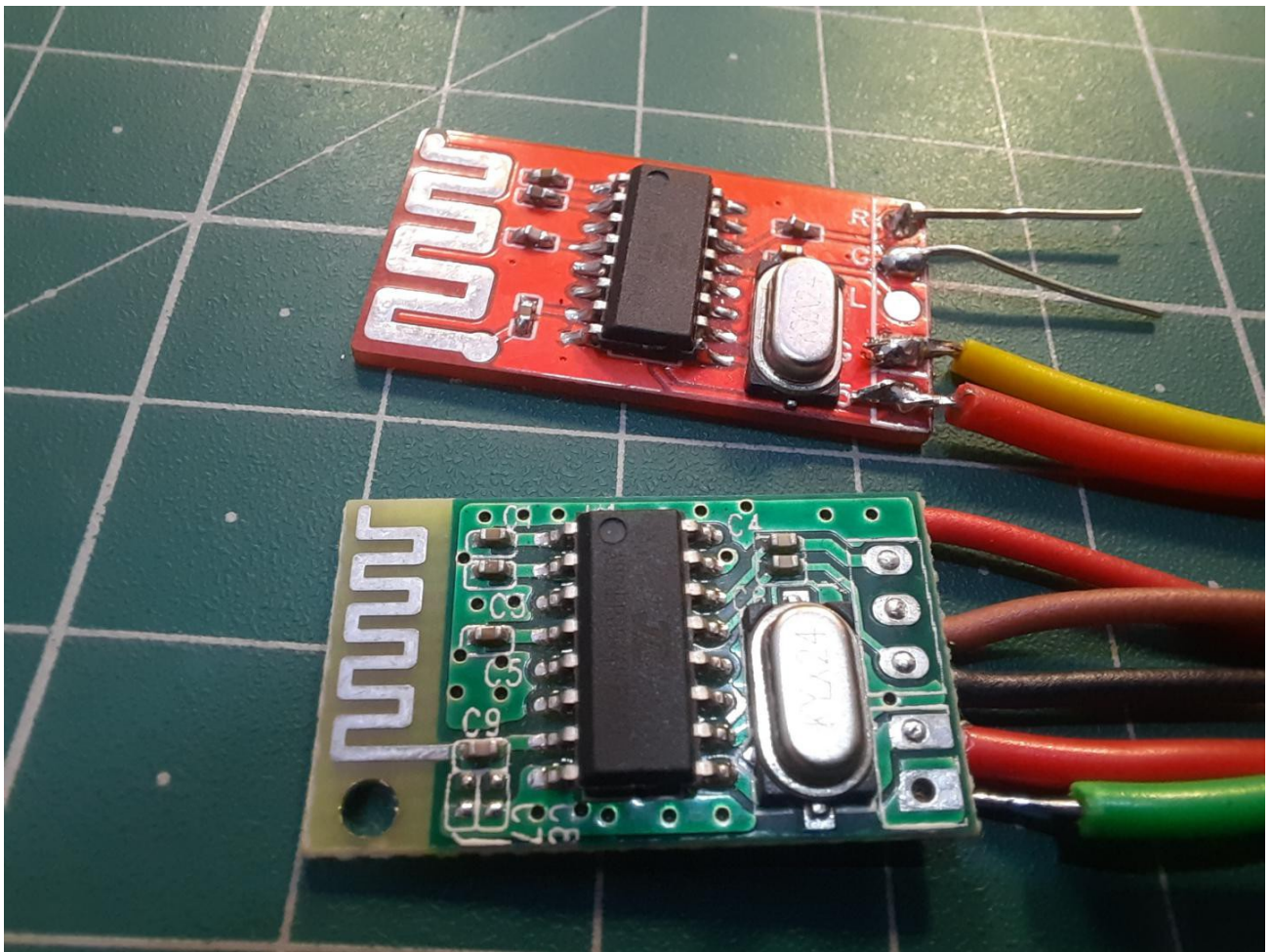**JL series Bluetooth chips (AC6939B\_SOP16):**



Nowadays, these are very popular, highly integrated and cheapest ICs with a lot of features. Available globally and manufactured in China, yet there is no any details or datasheets about them on web. I think manufacturer doesn't want to disclose the info.

**How I got Pinout and circuit:**

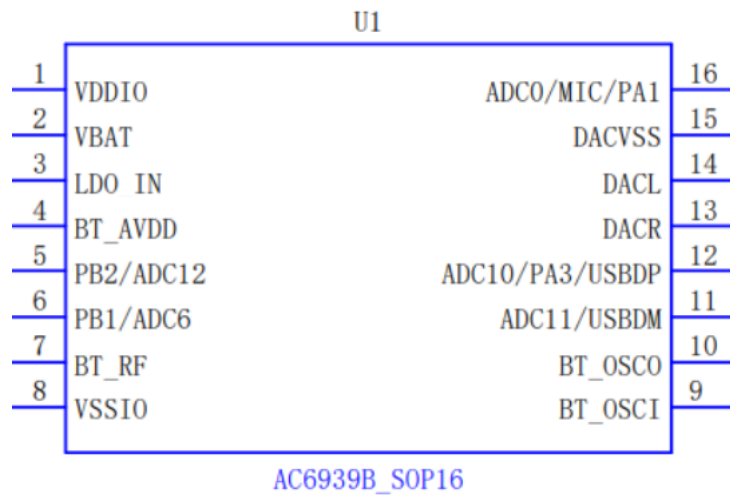

After searching the specific IC number with package details, SOP 16 pin. I found a website [chenbingdom.com](http://chenbingdom.com), that may give the pin details and circuit description about this JL series ICs. This website uses a http: unsecure connection, so make sure before you reach to them. All the PDF and datasheets are in Chinese language and provide only the schematics of the circuit. Which can be modified further as per requirements.

#### Features of my version chip (AC6939B\_SOP16):

- 1) Frequency range: 2402-2480 MHz
- 2) Modulation type: GFSK (Battery life saving technique)
- 3) Working voltage: 3.0 - 5.5volts
- 4) Low power consumption: 14mA @4volts
- 5) Low components used
- 6) Clock: 24 MHz Crystal
- 7) Stereo mode available
- 8) USB supported
- 9) Onboard Mic options
- 10) Led indicator mode available
- 11) AD Key supported (Increase/ Decrease volume and channels)
- 12) 10-meter range

#### Circuit Diagram:

This is circuit for chip 6939B, you can get specific IC pinout and schematics [from Here](#)

In the circuit 24MHz crystal oscillator is used without capacitors in series with it. Also, the SMD inductor is not mandatory to use. This ic supports dual channel audio out, so we can use this with stereo audio amplifier systems.

#### Modified circuit layout:

The real operating circuit do not need too many components, that's why I draw a simplified schematics by my own.

just ignore the IC pins and name. I am using ch340g in the schematics because this bluetooth IC is anonymous and package is same SOP16. You can see the Real pinout in above image from this. In case you want to modify anything you can [download](#) the Gerbers from here. If you want to use my layouts then open source link is here.

#### PCB layout:

After making a cool circuit, I designed the PCB in Easyeda and Order it from [JLCPCB](#). They are offering the PCB prototypes in cheapest. I got 30pcs of these small PCB with the thickness of 1.2mm and red color Hasl finishing just in \$5. [Download Gerber files from here.](#)

And here is a special offer for you guys, [Sign-up to JLCPCB using this link](#) and get free coupons worth \$27. Try their SMT assembly service to get rid of soldering and assembly process.

The ordering process is also quite simple, just follow these steps.

Go to JLCPCB> Upload Gerbers > Select quantity, color and surface finish> Add to cart > Checkout and receive package within 7 days.

Components needed:

- 1) AC6939B\_16\_SOP Bluetooth Ic
- 2) 24Mhz crystal
- 3) 100nf capacitor
- 4) 15 pf capacitors
- 5) Wires and connectors

Assembly:

I got all the components from the JL group of Bluetooth chip, I can't share the BOM officially as per their rules. Then I solder the 24Mhz crystal.

Then the main chip and some supported capacitors circuitry. All the work can be done using Hand soldering method, no need of special soldering machines.

I supplied the circuit with 5 volts and then tried to connect Bluetooth using mobile. Because this is using Bluetooth 3.0 so easy to pair with all devices except auto connect.

Checking the operation...

Read more »

View all details

FILES

Gerber\_PCB\_OWEN BT 3.0\_2022-03-24.zip

Zip Archive - 45.81 kB - 03/24/2022 at 17:43



Datasheet.pdf

Adobe Portable Document Format - 203.96 kB - 03/24/2022 at 17:43



CIRCUIT SCHEMATICS.png

Portable Network Graphics (PNG) - 77.01 kB - 03/24/2022 at 17:43



ENJOY THIS PROJECT?

Share



DISCUSSIONS

Log In or become a member to leave your comment

Log In/Sign up to comment



ricky el-qasem wrote 03/09/2023 at 10:54

When I inquired about buying the CHIP there was some question about firmware. Is this necessary?



vladlen wrote 03/25/2022 at 16:51

Your antenna isn't antenna cause awful designed.



Per Jensen wrote 04/01/2022 at 21:14

Yeah, it will have a pretty poor performance. The groundplane under the antenna won't help either. But i've seen worse.

---

#### SIMILAR PROJECTS



Arduino based Digital Audio FM Radio using RDA5807




Sagar 001

# MOSQUITO REPELLENT CIRCUIT




Mosquito Repellent circuit using 555 timer

 ElectroBoy

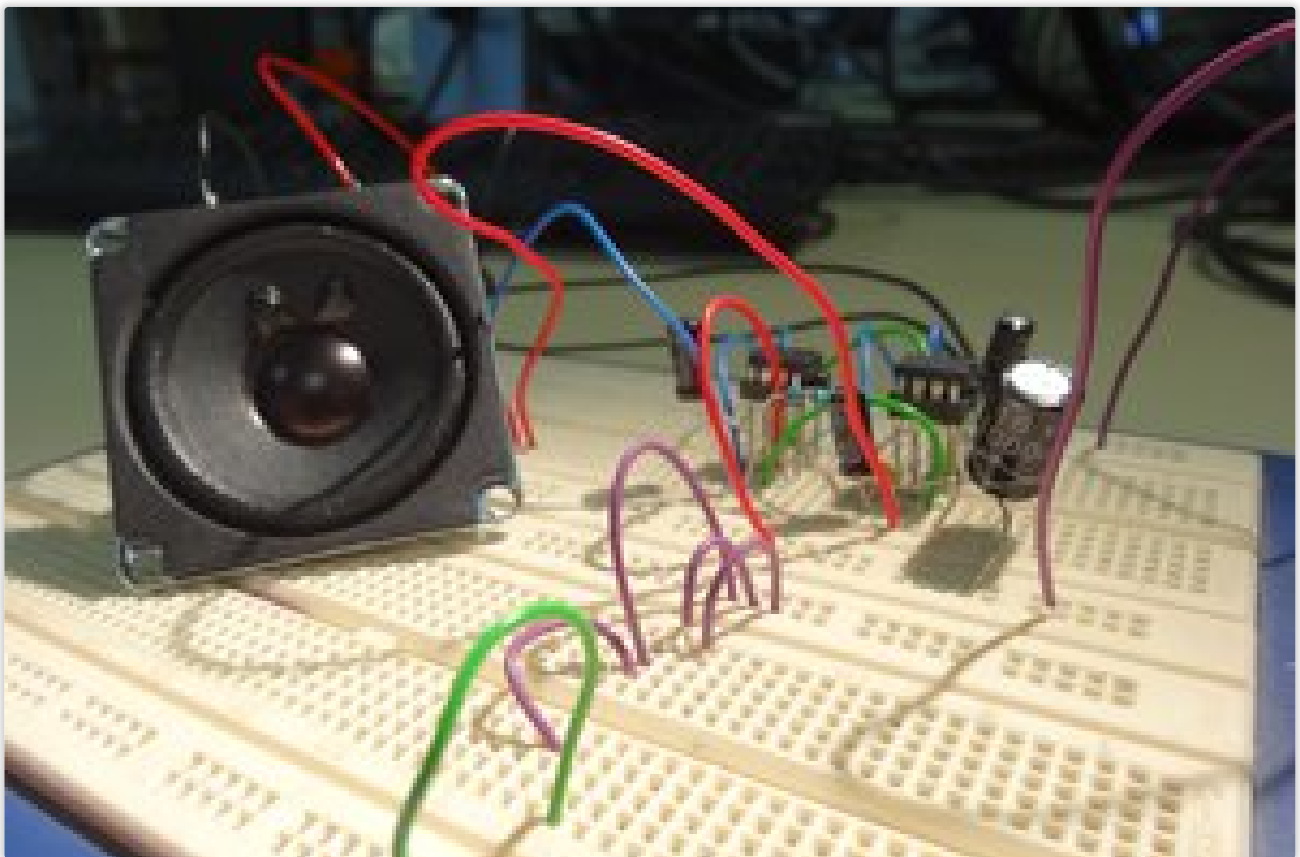


Portable Stereo Speaker

 Aymeri

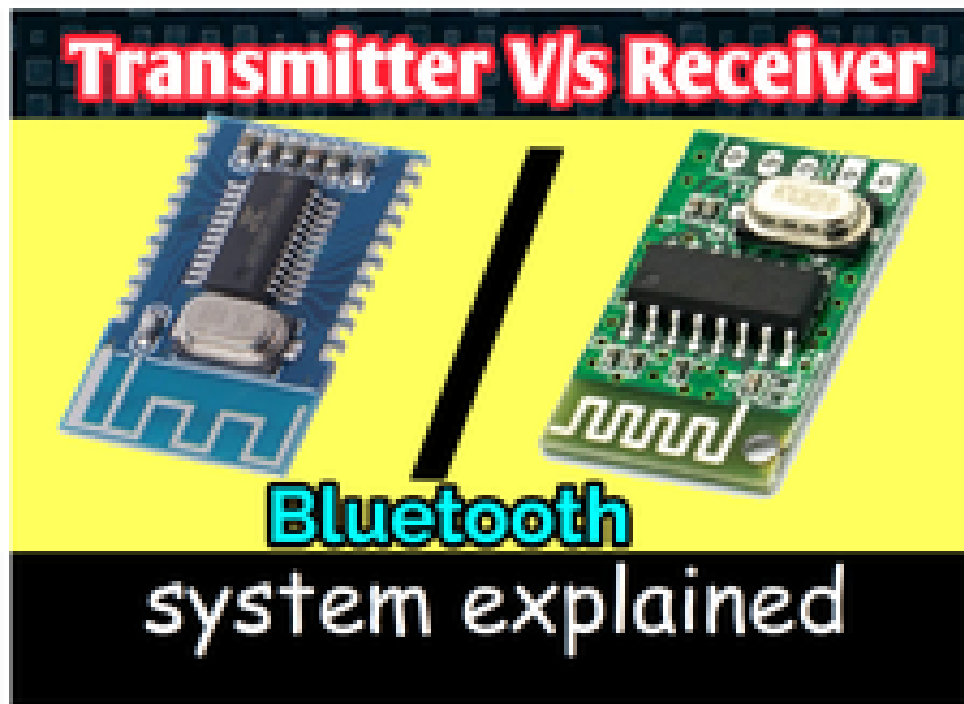

Bluetooth Transmitter – Chipset, Power, Datasheet

 Sagar 001

Does this project spark your interest?

Become a member to follow this project and never miss any updates

Your email address

Password

Enter captcha



Become a member

↑ Going up?

[About Us](#)

[Contact Hackaday.io](#)

[Give Feedback](#)

[Terms of Use](#)

[Privacy Policy](#)

[Hackaday API](#)

© 2023 Hackaday